

# Simple Battery Charge Level Indicator – Green for >10V (Charged), Red for ≤10V (Low)

## How It Works

This is a low-component battery voltage level indicator circuit that visually shows whether a battery is adequately charged or running low.

When the battery voltage is above ~10 V the 10 V zener diode breaks down in reverse and supplies base current to transistor Q1.

→ Q1 turns on, pulling current through the green LED (D1) → green light indicates "battery is good / sufficiently charged".

When the battery voltage drops below ~10 V, the zener no longer conducts significantly → Q1 turns off.

→ The base of transistor Q2 now receives current through R2 (and the path involving the green LED), turning Q2 on.

→ Current flows through the red LED (D2) and R3 → red light indicates "battery low / needs recharging".

The circuit uses a clever transistor inverter configuration so that only one LED is clearly lit at a time (the other is either off or light a bit). It draws very little current and works well for monitoring 9–12 V battery systems.





